

Buck Converter using voltage mode control


Presented to: Dr. A.V. Raviteja

MOHD ANAS KHAN

MANISH PANT




Parameters of Buck Converter

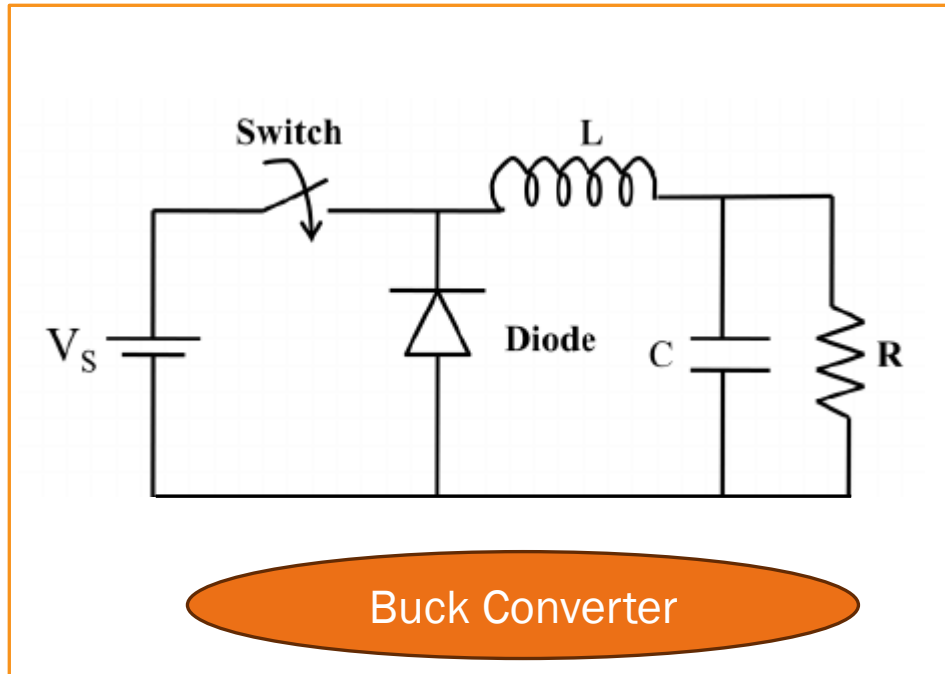

Name of parameter	Value of parameter
V_S	30 V
f_{sw}	20 kHz
L	10 mH
C	1000 μF
R	100 Ω
V_o	15 V


Fang, J. & Tsai, Sheng-Hong & Yan, Jun-Juh & Chen, P. & Guo, Shu-Mei. (2021). Realization of DC-DC Buck Converter Based on Hybrid H2 Model Following Control. IEEE Transactions on Industrial Electronics. PP. 1-1. 10.1109/TIE.2021.3062268.

Schematic of simulation model

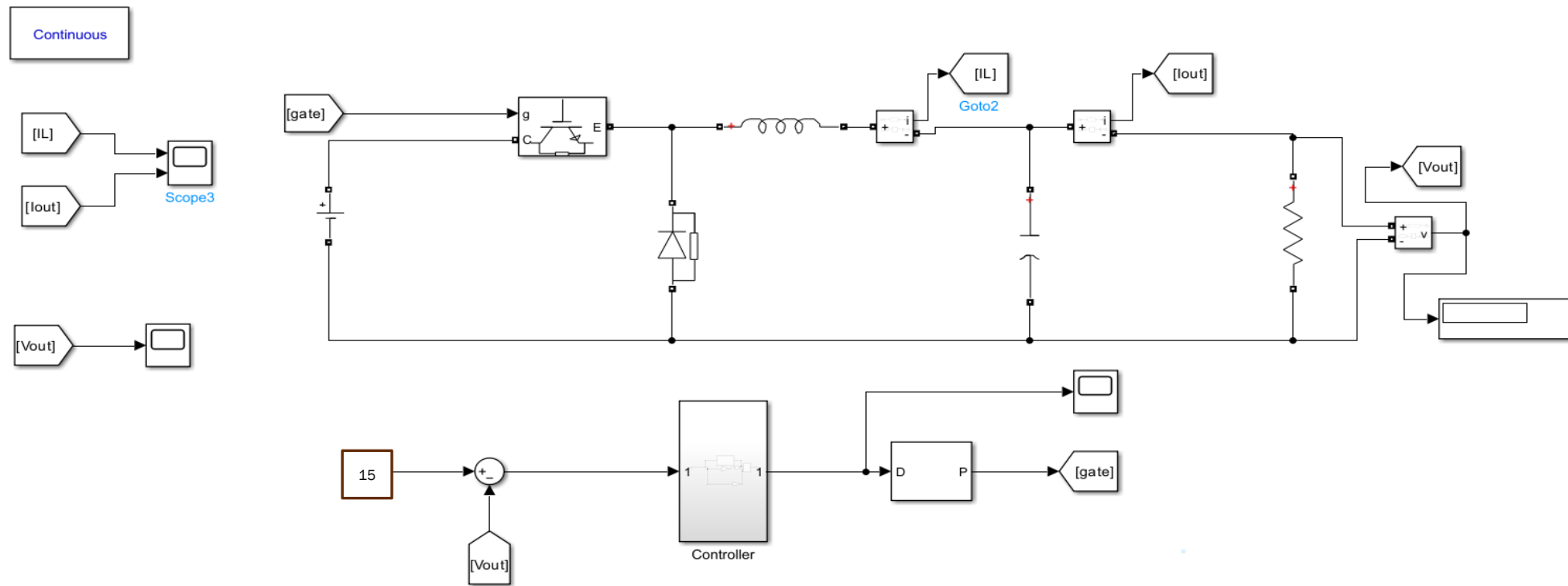


Voltage mode controlled buck converter

Controller

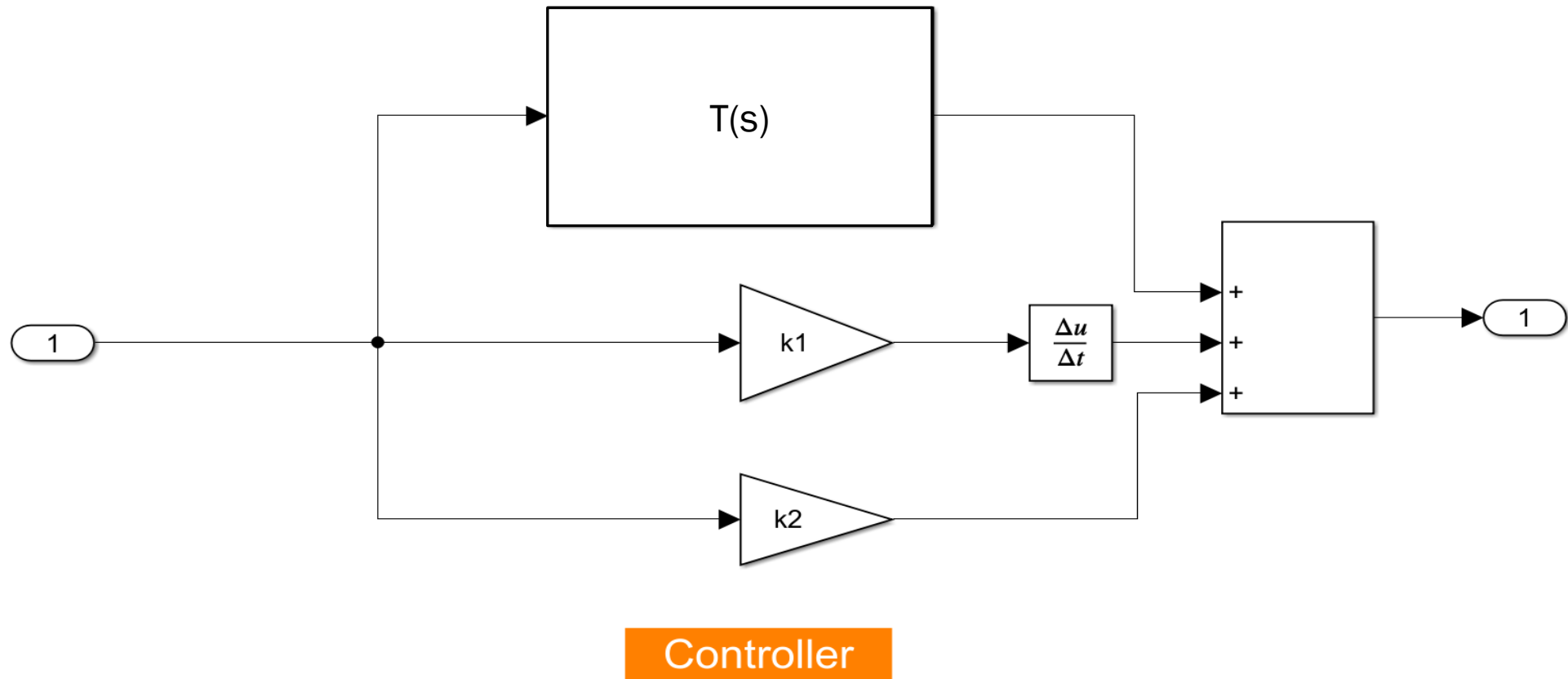

Output Voltage and Ref Voltage

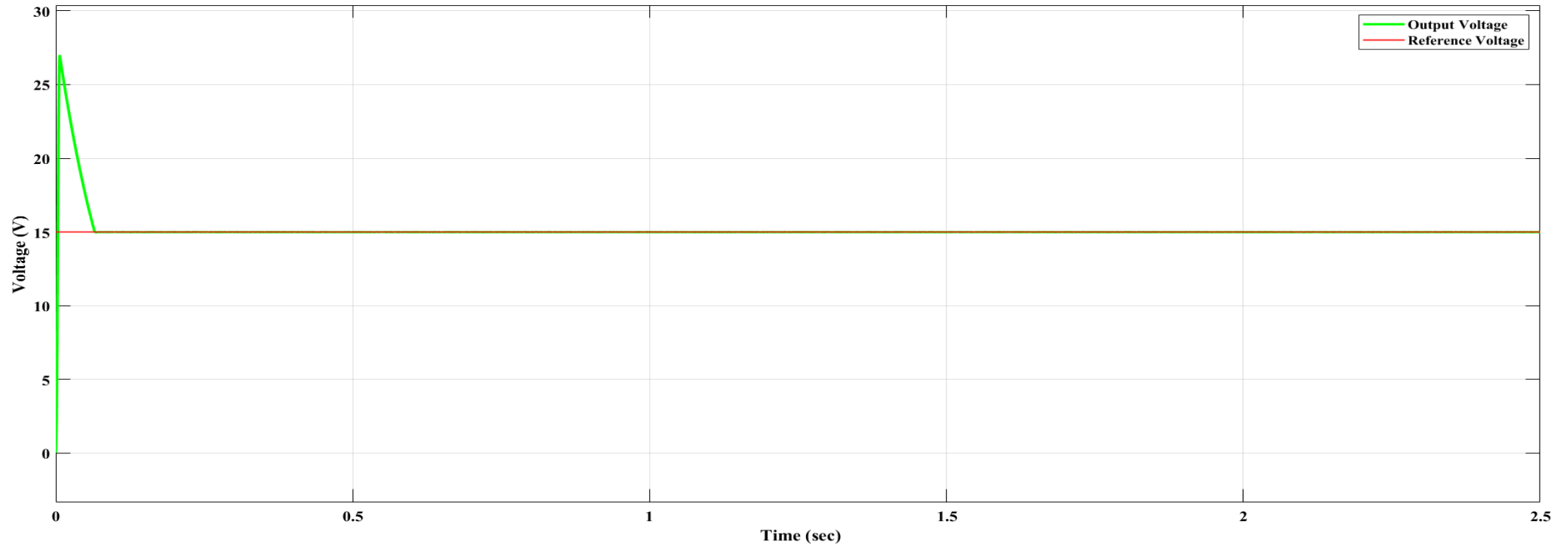

Transfer functions

Converter transfer function:

$$G1(s) = \frac{3000000}{s^2 + 10s + 1000000}$$


Controller transfer function:

$$G2(s) = \frac{s^2 + 2900s + 1800000}{90s + 60000}$$


Open loop transfer function:

$$G(s) = G1(s) * G2(s) = \frac{3000000s^2 + 8700000000s + 540000000000}{90s^3 + 60900s^2 + 90600000s + 60000000000}$$



Bode plots

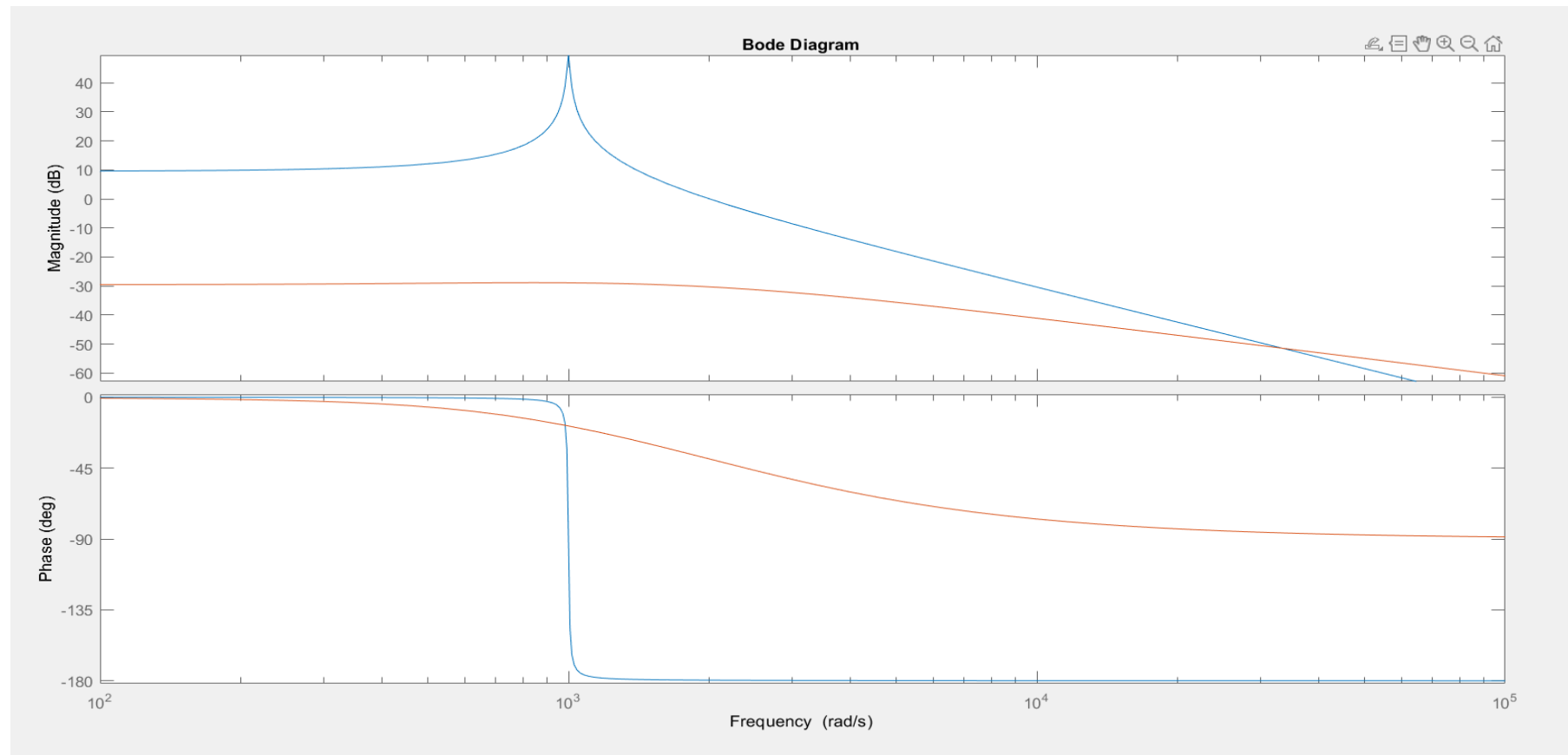

Bode plot of system with controller

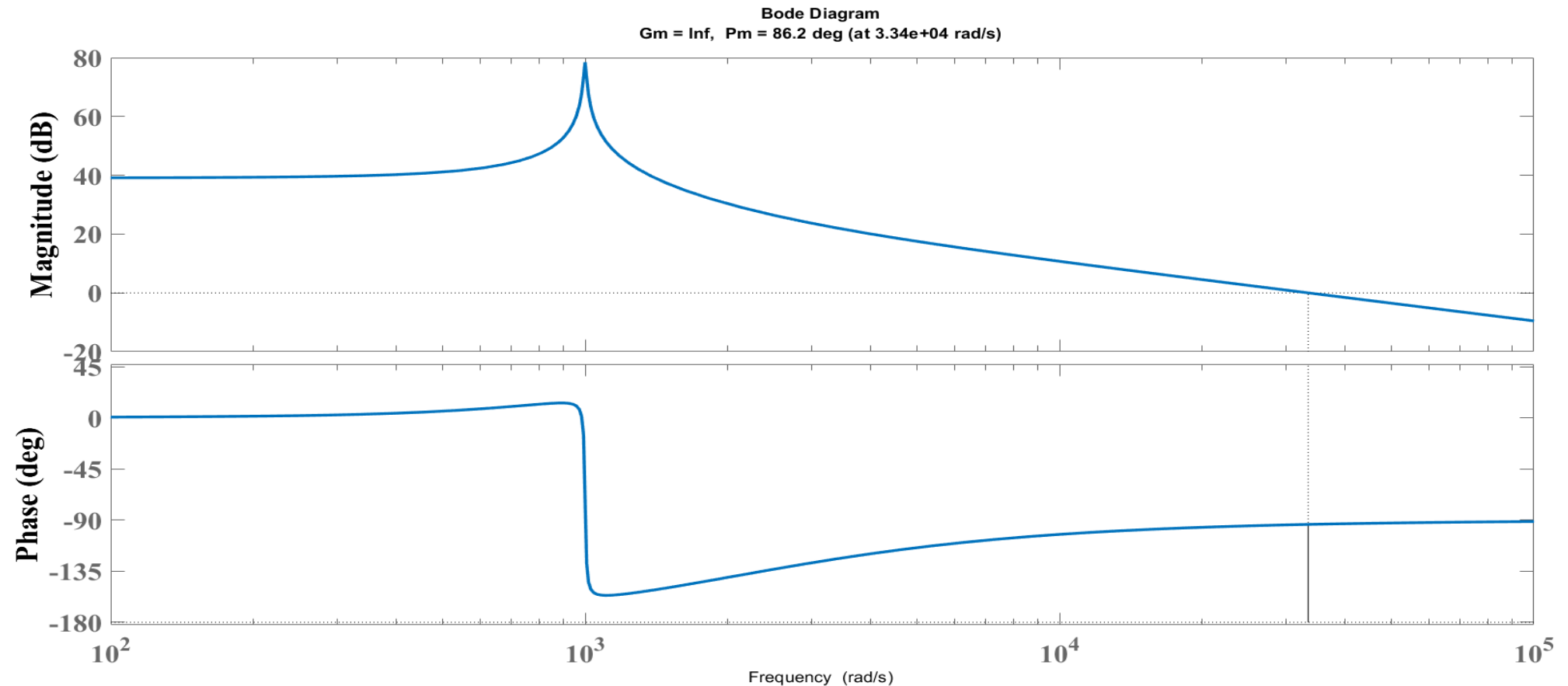

Nyquist plot

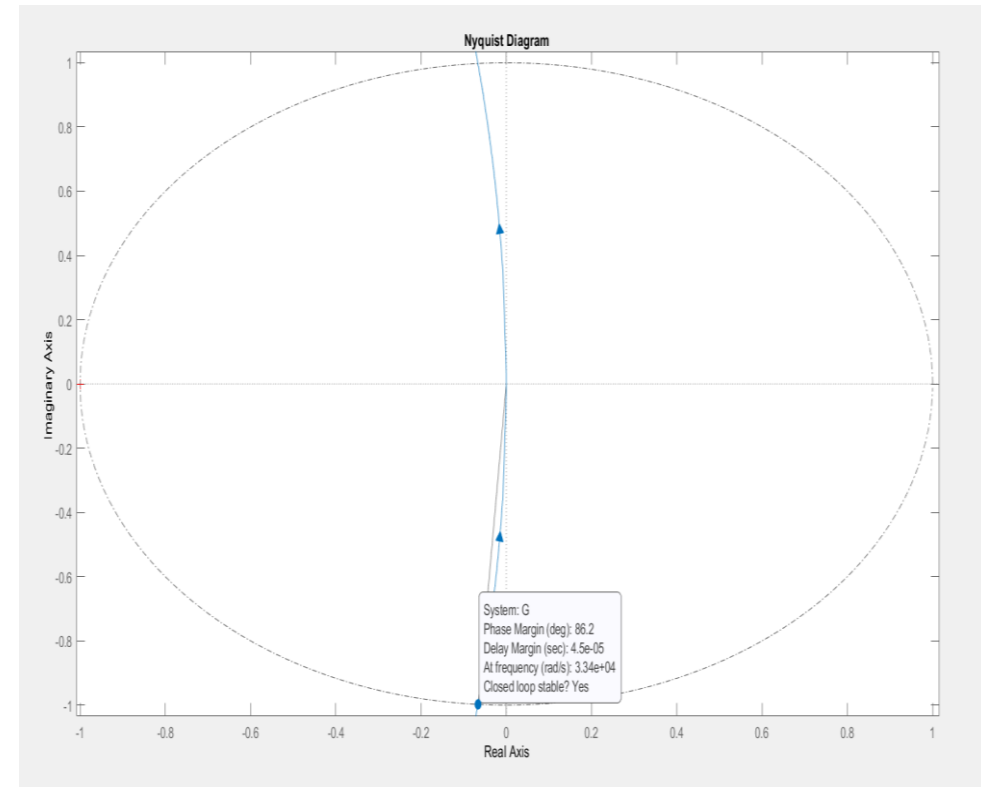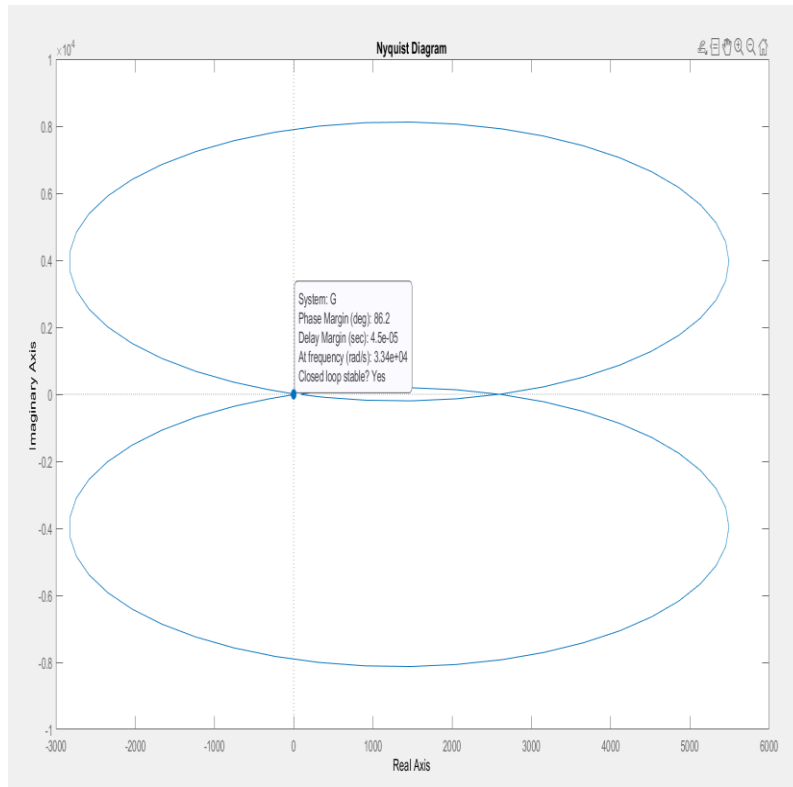


Transfer function with esr

$$G2(s) = \frac{s^2 + 2900s + 1800000}{90s + 60000}$$


$$\frac{V_o}{d} = \frac{V_{in}(1 + s * r * C) * G_c}{L * C * \left(s^2 + s \left(\frac{1}{R * C} + \frac{r}{L} \right) + \frac{1}{L * C} \right)}$$

$$M(s) = \frac{100 * s^3 + 29030 * s^2 + 1.802 * 10^8 * s}{3 * s^3 + 102030 * s^2 + 2.903 * 10^8 * s + 1.802 * 10^{11}}$$



Root locus

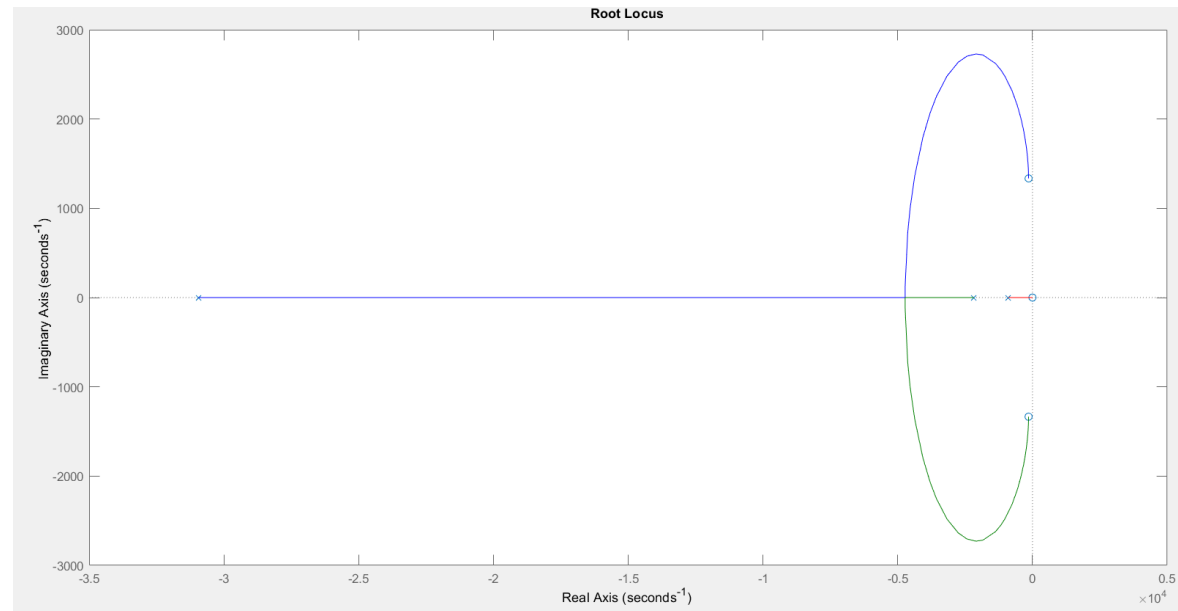


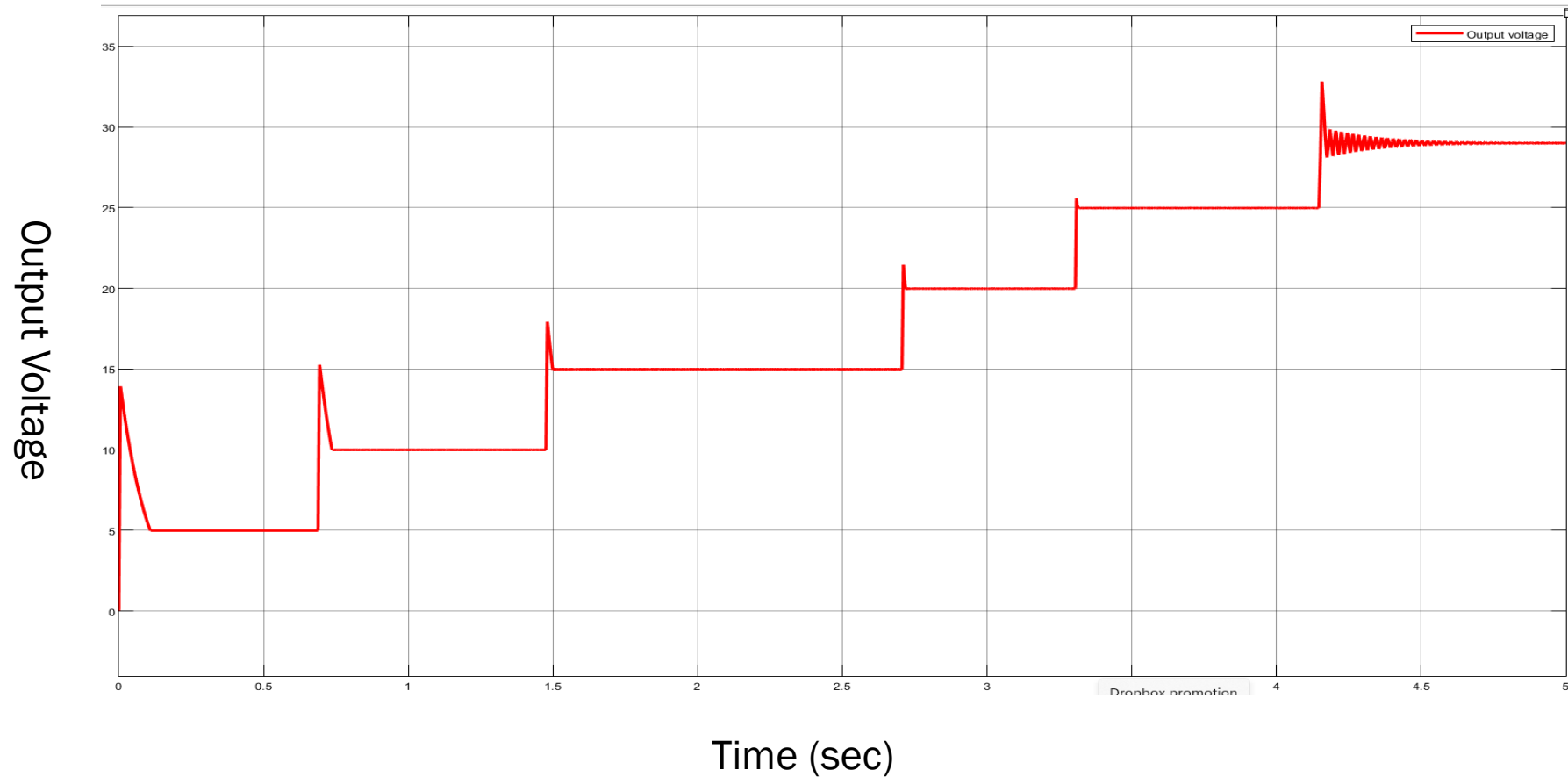
Output Voltage waveforms for different values of Ref Voltage





Output voltage variation with resistance

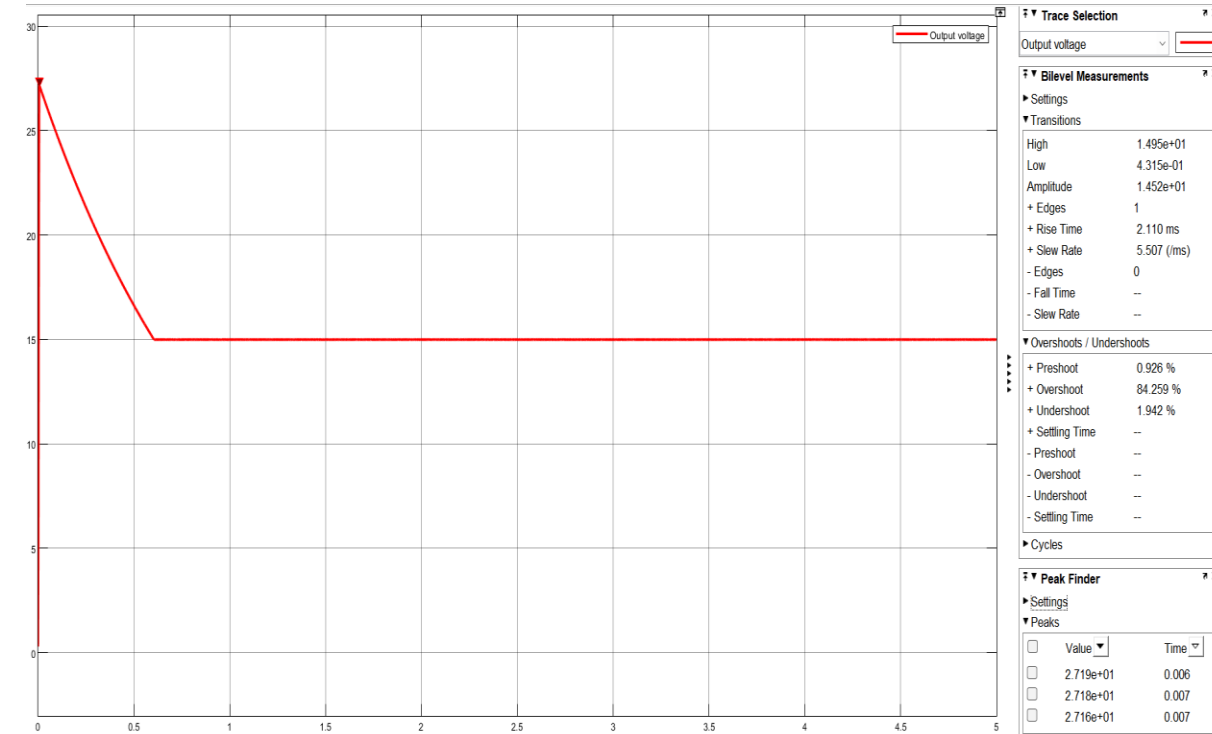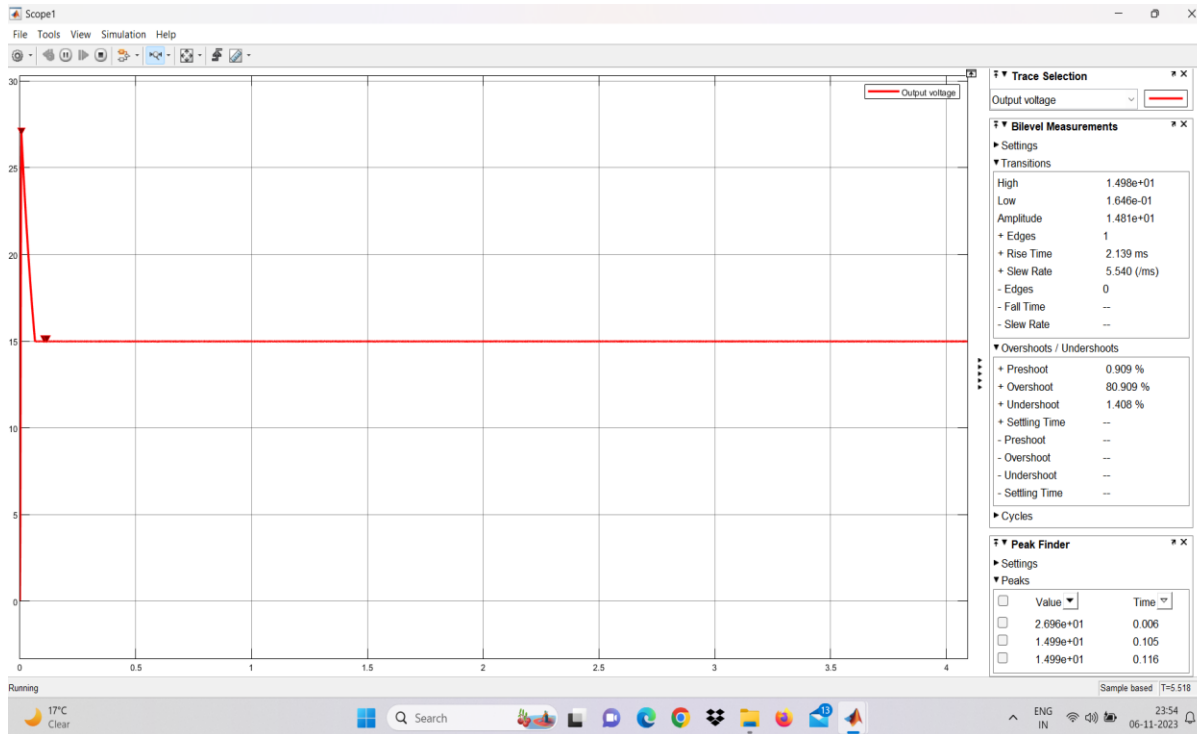

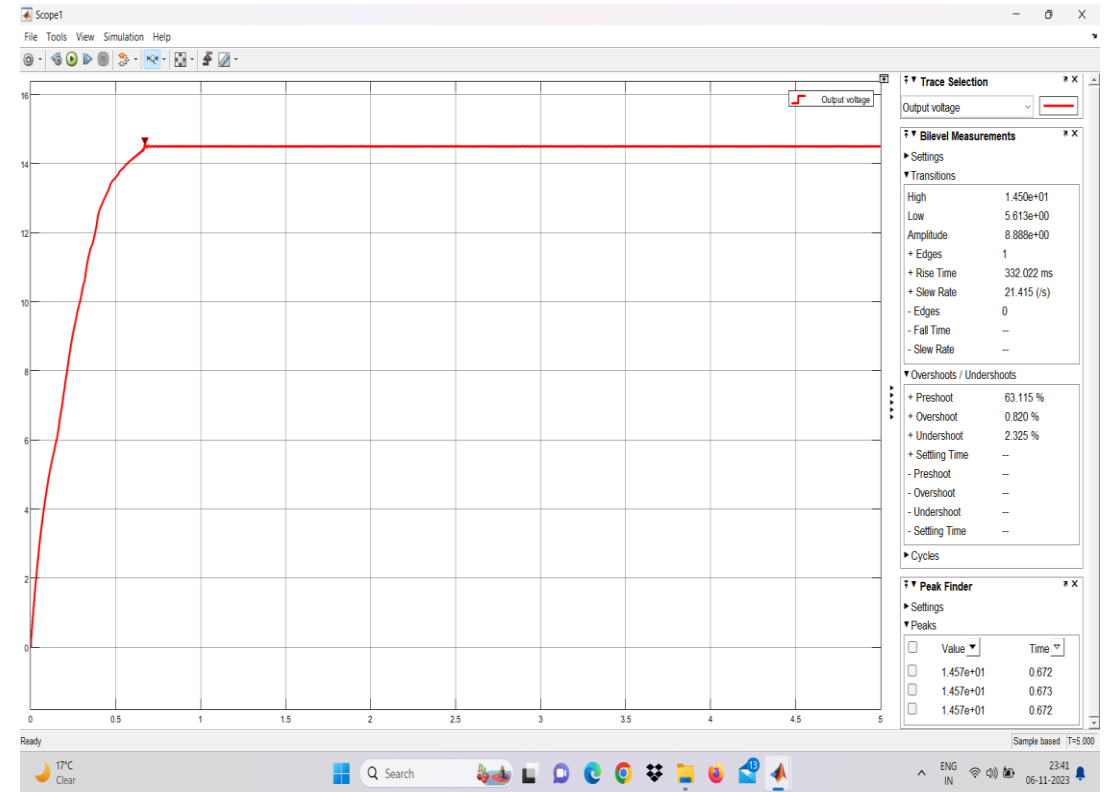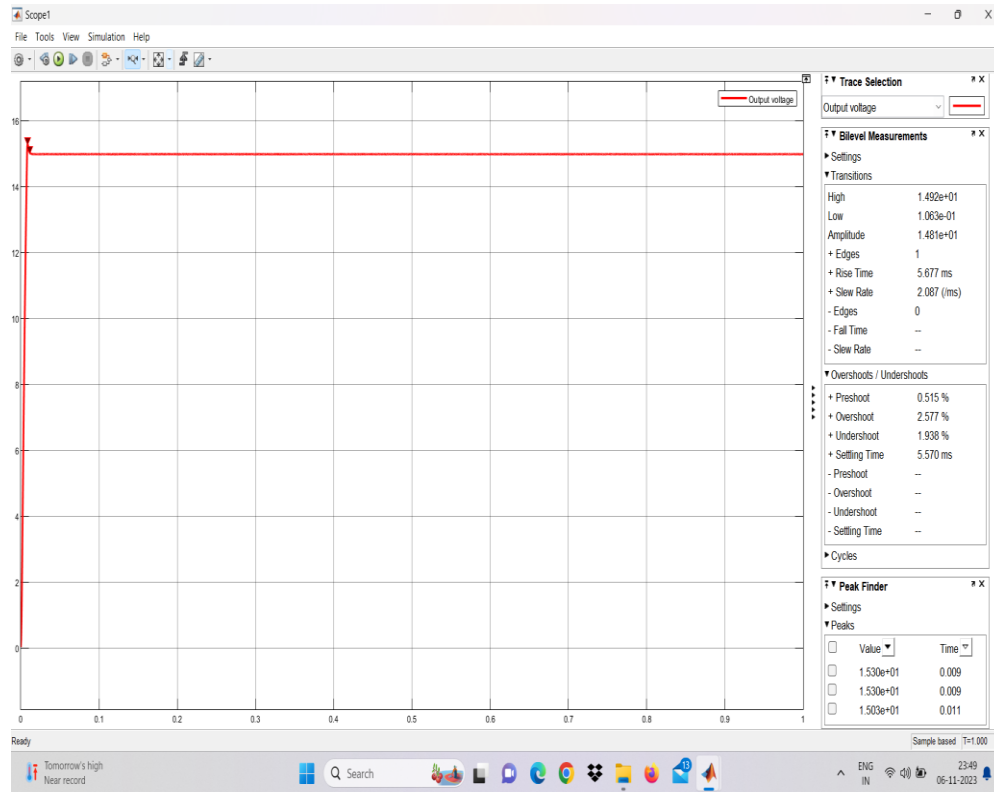Output voltage variation with inductor resistance



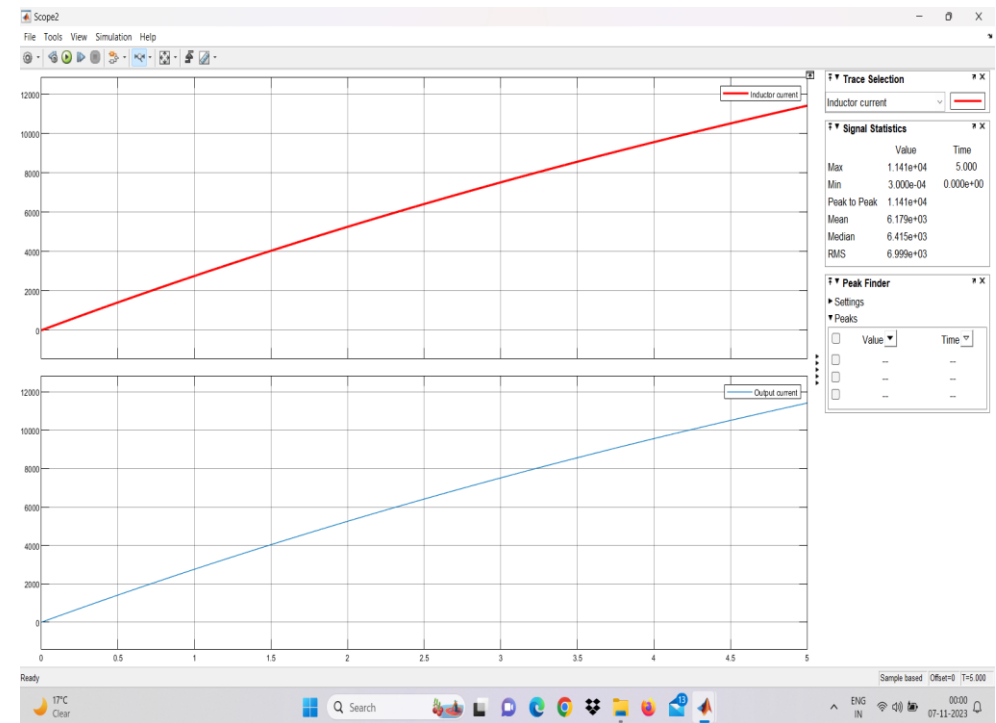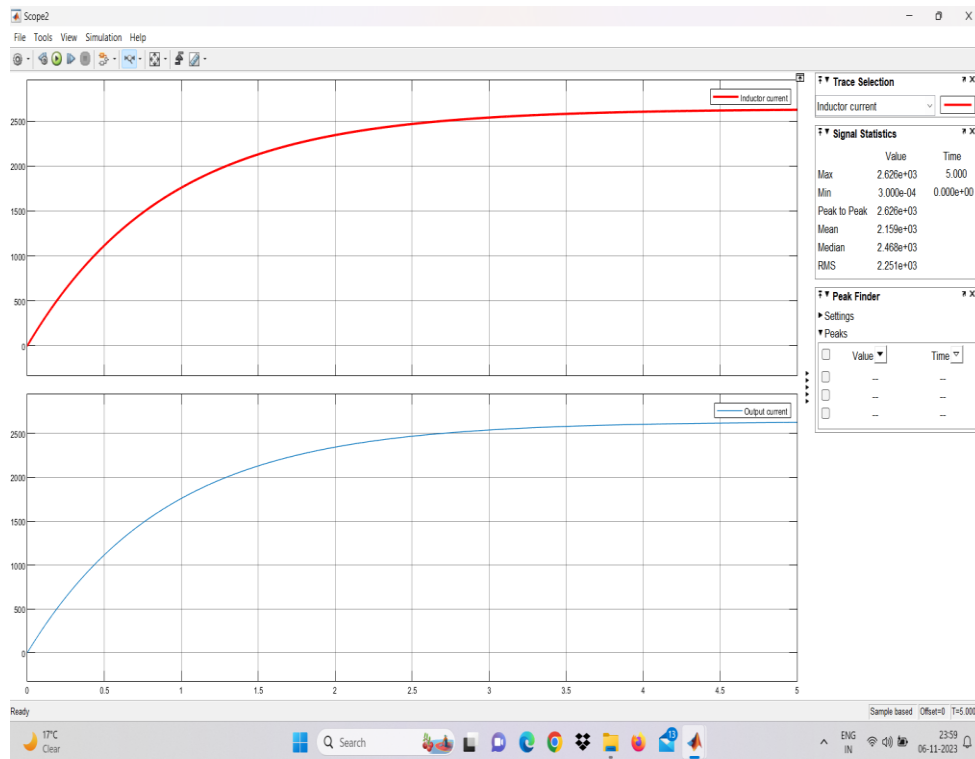Inductor and output current during short circuit condition



EXPLANATIONS OF QUESTION ASKED DURING PRESENTATION

Q.) What is the reason behind increase in rise time with increase in ESR of inductor?

A.) An increase in ESR increases the value of damping ratio which in turn reduces the value of rise time according to the following formula.

$$t_r = \frac{\pi - \theta}{\omega_n \sqrt{1 - \zeta^2}}$$

Thank You